
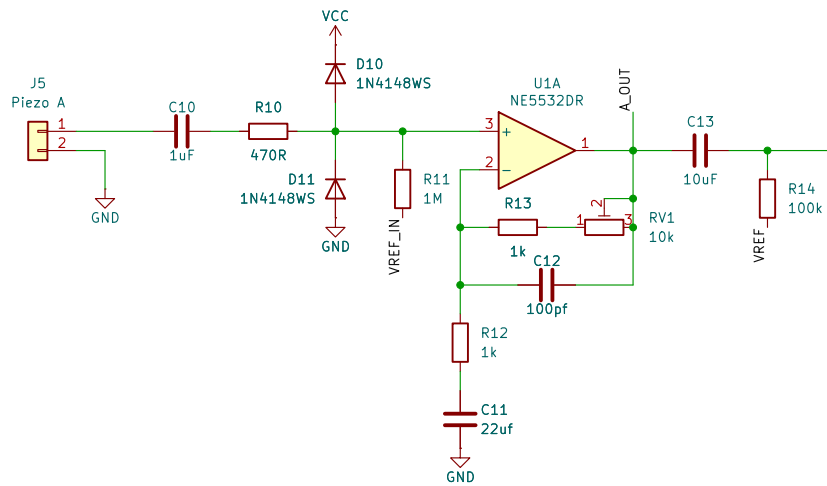


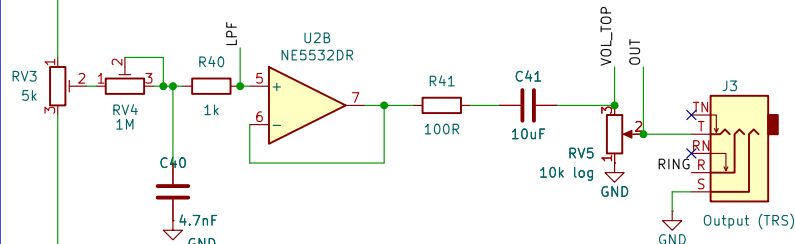PREAMP A (gain = 1 + (R13+RV1)/R12 = x2...x12, CW = more gain)




BLEND (RV3) -> HIGH-CUT LPF (RV4) -> BUFFER -> MASTER (RV5)




Low pass filter $f_c = 1 / (2 \pi (RV4 + \text{blend source}) C40) = 27 \text{ kHz} \dots 34 \text{ Hz}$
If you want to wire the filter as a pot you intend to control, find an log taper one because the linear ones will have a really small usable range (fine for trim)
Volume pot works okay as linear, but log is better!

PREAMP B (identical to A, gain trim RV2)

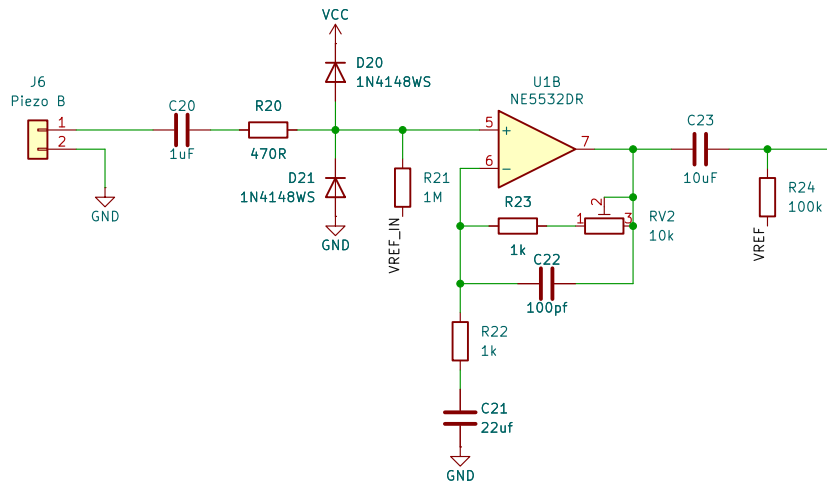


PHASE INVERT

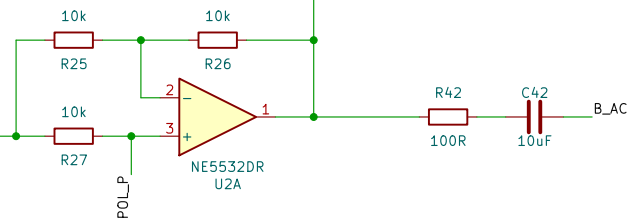

An extra inverting opamp stage flips the signal from preamp B when engaged (SW2-1 turns it on / off)

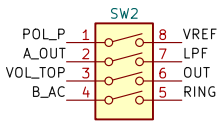SW2 MODE / POLARITY DIP (set with power off)




Mode / Polarity

There's some fuckery here so that it can be wired for mono, or for stereo (Stereo bypasses everything after and including the blend)

MONO blend -> low-cut -> volume -> tip (TS or TRS lead): 2 OFF, 3 OFF, 4 OFF
STEREO A -> tip, B -> ring, no blend/filter/volume (TRS lead): 2 ON, 3 ON, 4 ON
1 = B polarity 2 = A direct 3 = volume bypass 4 = B to ring

POWER

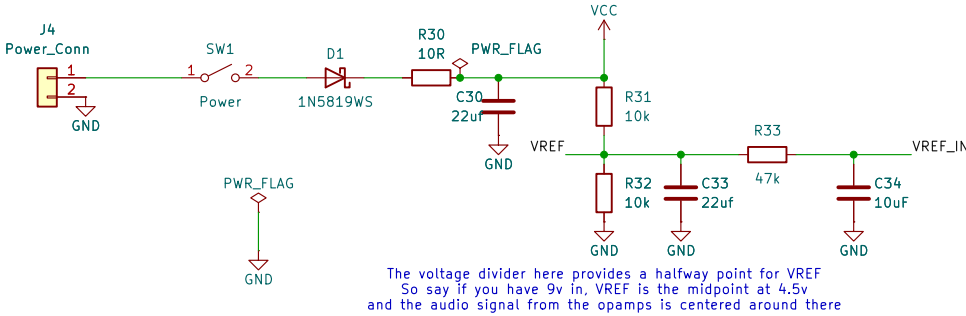

The voltage divider here provides a halfway point for VREF
So say if you have 9v in, VREF is the midpoint at 4.5v
and the audio signal from the opamps is centered around there

OP-AMP SUPPLIES

